

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)
BSc DEGREE EXAMINATION DECEMBER 2018
(Fifth Semester)
Branch - PHYSICS

PRINCIPLES OF DIGITAL ELECTRONICS

Time : Three Hours

Maximum : 75 Marks

SECTION-A (20 Marks!)

Answer ALL questions

ALL questions carry EQUAL marks (10x2 = 20)


- 1 State Demorgan's theorems.
- 2 Give the symbol and truth table for AND gate.
- 3 Deduce 2-input multiplexer.
- 4 Write the difference between a demultiplexer and a decoder.
- 5 Subtract $(14)_{10}$ from $(17)_{10}$ using 1's complement and 2's complement method.
- 6 Draw the circuit diagram for RS Flip flop and give its truth table.
- 7 What is a ring counter? Draw the logic diagram of a ring counter.
- 8 Differentiate asynchronous and synchronous counters.
- 9 What are PROM and EPROM?
- 10 Write a note on binary ladder.

SECTION - B (25 Marks)

Answer ALL Questions

ALL Questions Carry EQUAL Marks (5x5 = 25)

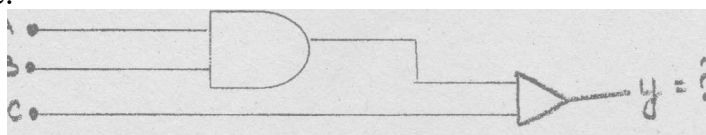- 11 a Obtain the logic expression for the given logic circuit and form the truth table.



OR

- b Simplify using Karnaugh map
 $Y = F(A, B, C, D) = \Sigma (0, 1, 2, 4, 5, 10, 11, 14, 15)$.

- 12 a What is an ASCII code? What is the ASCII code string for the word "HELLO"?

OR

- b $(29A.8)_{16} = (x)_{10} = (y)_2 = (z)_8$ Find x, y & z.

- 13 a What are flip-flops? Explain the working of RS flip-flop with diagram.

OR

- b Explain the working of adder and subtractor circuits.

- 14 a Explain the function of a synchronous counter with logic circuit diagram.

OR

- b Describe Mod-5 counter with necessary diagram.

Cont...

15 a Discuss with necessary block diagram, the working of a counter type A/D converter.

OR

b Explain briefly the evolution of ROM's and RAM's.

SECTION - C (30 Marks)

Answer any **THREE** Questions

ALL Questions Carry **EQUAL** Marks (3 x 10 = 30)

16 i) Obtain SOP expression using K-map $F(A, B, C, D) = \sum(0, 3, 4, 7, 8) + I_d$
(10, 11, 12, 13, 14, 15).

ii) Obtain POS expression using K-map
 $F(A, B, C, D) = \prod(0, 1, 2, 3, 4, 10, 11)$.

17 What are multiplexers? Explain 1 to 16 decoder with diagram.

18 Explain in detail the working of a master slave JK flip flops with diagram.

Describe the serial in-serial out and serial in parallel out and parallel in serial out shift registers.

20 Explain with circuit diagram, the working of a resistor ladder D/A converter. Give the necessary theory.

Z-Z-Z

END