

**PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)**

**BSc DEGREE EXAMINATION MAY 2017 !5cTuo2.
(First Semester)**

Branch- **COMPUTER TECHNOLOGY**

DIGITAL ELECTORNICS

Time : Three Hours

Maximum : 75 Marks

SECTION-A (20 Marks)

Answer **ALL** questions

ALL questions carry **EQUAL** marks (10 x 2 = 20)

- 1 Convert the binary number 100101_2 to decimal number.
- 2 Give the use of BCD code.
- 3 Give the truth table for NOR gate.
- 4 State any two applications of XOR gate.
- 5 Define maxterms.
- 6 Define canonical form.
- 7 Define Half-adder.
- 8 Define the term decoder.
- 9 What are the two categories of MSI counter?
- 10 Define registers.

SECTION - B (25 Marks)

Answer **ALL** Questions

ALL Questions Carry **EQUAL** Marks (5 x 5 = 25)

- 11 a Convert the binary number 1010.011 to decimal, octal and hexadecimal.
OR
b Perform the following operation in the given numbers :
(i) Binary Addition : $101111 + 100101$
(ii) Binary Subtraction : $1110011 - 100011$
Check using decimal values.
- 12 a Discuss about Exclusive OR and Exclusive NOR gates.
OR
b Explain Integrated circuits.
- 13 a Express the Boolean function $F = A + B' C$ in a sum of m interms.
OR
b Explain De-morgan's theorem.
- 14 a Explain Full-Adder.
OR
b Explain Encoders.
- 15 a Explain Master Slave flip-flop.
OR
b What are counters? Write a note on Ripple counter.

SECTION - C (30 Marks)

Answer any **THREE** Questions

ALL Questions Carry **EQUAL** Marks (3 x 10 = 30)

- 16 Give a detailed view on number systems.
- 17 Explain the various logic gates with its truth table in detail.
- 18 Write the basic theorems and properties of Boolean Algebra. Prove theorems relates to Commutative and Associative Law.
- 19 Explain multiplexers and demultiplexers.
- 20 Discuss the different types of flip flops in detail.