

**PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)**

**BSc DEGREE EXAMINATION MAY 2017
(Fifth Semester)**

Branch- **PHYSICS**

PRINCIPLES OF DIGITAL ELECTRONICS

Time : Three Hours

Maximum : 75 Marks

SECTION-A (20 Marks)

Answer **ALL** questions

ALL questions carry **EQUAL** marks (10 x 2 = 20)

- 1 Give the truth table and Boolean expression for a two input i) OR gate and ii) the AND gate.
- 2 Prove that $A + A B = A + B$.
- 3 Convert $(52)_{10}$ to its equivalent binary number.
- 4 Convert $(45.6)_8$ to decimal.
- 5 Calculate $(-21)_{10}$ using 2's complement arithmetic method. *
- 6 a) Add the binary 1011 and 1001 (b) Subtract the binary 1101 from 1111.
- 7 What is a shift register? Give any two uses of it.
- 8 What is meant by asynchronous counter?
- 9 What are ROM and RAM?
- 10 Give any two difference between D / A and A/D converters.

SECTION - B (25 Marks)

Answer **ALL** Questions

ALL Questions Carry **EQUAL** Marks (5 x 5 = 25)

- 11 a ' State and prove Demorgan's theorems.
OR
b Simplify the expression $Z = A BC + AB C + ABC + ABC$
implement the result using NAND gates.
- 12 a Explain the operation of a seven segment decoder.
OR
b Describe the function of a Demultiplexer.
- 13 a What is Schmitt trigger? Explain how Schmitt trigger could be constructed using op amp? Obtain an expression for its hysteresis voltage.
OR
b Describe the construction, working and use of D flip flop. Give its truth table.
- 14 a Describe the Mod 3 counter with necessary diagram.
OR
b Draw the circuit of a ring counter and discuss its working.
- 15 a Explain the simultaneous method of A/D conversion.
OR
b Write a note on variable resistor network.

SECTION - C (30 Marks)

Answer any **THREE** Questions

ALL Questions Carry **EQUAL** Marks (3 x 10 = 30)

- 16 Using Karnaugh map, simplify the Boolean function.
 $F = \sum m(0, 1, 2, 3, 11, 12, 14, 15)$ Implement the result using logic gates.
- 17 Explain the Excess —3 code and the Gray code with examples.
- 18 Explain, the action of JK flip flop, giving truth table. What are its drawbacks? What is meant by toggling?
- 19 Discuss the serial in parallel out and parallel in parallel out shift registers.
- 20 Explain with relevant diagram the function of binary ladder type D/A converter