

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)

BSc DEGREE EXAMINATION DECEMBER 2017
(First Semester)

Branch COMPUTER TECHNOLOGY

DIGITAL ELECTRONICS

Time : Three Hours

Maximum ; 75 Marks

SECTION-A (20 Marks)

Answer ALL questions

ALL questions carry EQUAL marks (10x2. = 20)

- 1 Convert the binary number $(1010.011)_2$ to decimal number system.
- 2 What is the main advantage of 8421 code?
- 3 Name the basic gates.
- 4 Give the truth table of NOR gate.
- 5 Symbol of sum term.
- 6 What is a K-map?
- 7 What is a full adder?
- 8 Define a decoder.
- 9 How can a JK FF be converted to a TFF?
- 10 What is the other name for asynchronous counter?

SECTION - B (25 Marks)

Answer ALL Questions

ALL Questions Carry EQUAL Marks (5 x 5 = 25)

- 11 a Working operation of Binary multiplication of given numbers
 $(11.110)_2$ by $(100.1)_2$.
OR
b Write short notes on Binary codes.
- 12 a With the truth tables and graphical symbols explain the universal gates.
OR
b Write a short note on integrated circuits.
- 13 a Simplify $Y = AB + ABC + A\bar{B} + A\bar{B}C$ using canonical method.
OR
b State and prove De Morgan's theorem.
- 14 a Write short notes on half subtractor.
OR
b Write short notes on Demultiplexer.
- 15 a Explain the working of a D-Flipflop.
OR
b Write short note on clocks.

SECTION - C (30 Marks)

Answer any THREE Questions

ALL Questions Carry EQUAL Marks (3 x 10 = 30)

- 16 Briefly explain about error detecting and error correcting codes.
- 17 Discuss the various applications of XOR gate.
- 18 Simplify the Boolean function using K-Map
 $f(A, B, C, D) = \sum (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
- 19 Explain about 8 to 1 line multiplexer with logic diagram, logic circuit and truth table.
- 20 Write in detail about clocked RS flip flop and clocked JK flip flop.