

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)

BSc DEGREE EXAMINATION DECEMBER 2017
(Third Semester)

Branch - **ELECTRONICS**

DIGITAL PRINCIPLES & APPLICATIONS

Time : Three Hours

Maximum : 75 Marks

SECTION-A (20 Marks)

Answer **ALL** questions

ALL questions carry **EQUAL** marks

(10 x 2 = 20)

- 1 Define Excess - 3 code.
- 2 What is the binary number for decimal (19) to?
- 3 Give the truth table for 2 inputs AND gate.
- 4 What is SOP?
- 5 Add $(111\ 1)_T$ and $(1010)_2$.
- 6 Define Decoder.
- 7 What are the types of Shift Register?
- 8 Draw the state diagram of mod 3.
- 9 State one main advantages of successive approximation method.
- 10 Define Accuracy.

SECTION - B (25 Marks)

Answer **ALL** Questions

ALL Questions Carry **EQUAL** Marks (5 x 5 = 25)

- 1 i a Convert (107.6875) to its equivalent binary number.
OR
b Explain the procedure for excess - 3 addition with an example.
- ! 2 a Using Boolean algebra show that
$$ABC + ABC + ABC + ABC = AB + BC + CA$$

OR
b Show that NAND is a universal gate.
- 13 a Explain half subtractor with its circuit and truth table.
OR
b Use 2's complement method to perform $M - N$ with $M = 1000100$ and $N = 1010100$.
- 14 a What is racing in JK flip flop?
OR
b Describe the working of ring counter.
- 15 a With a block diagram, explain the principle of A/D converter.
OR
b Explain the working of dual slope ADC with suitable block diagram.

SECTION - C (30 Marks)

Answer any **THREE** Questions

ALL Questions Carry **EQUAL** Marks (3 x 10 = 30)

- 16 Find X :
(i) $(72905)_{10} = X_{16}$ (ii) $(1011110100011000111)_2 = X_8$ (iii) $(3674)_8 = X_2$
(iv) $(10111)_2 = X_{10}$ (v) $(2\ C\ 9)_{16} = X_{10}$ (vi) $(0.372)_{10} = X_2$
- 17 Simplify the following Boolean function, using five variable maps :
 $F(A,B,C,D) = \sum(0,2,5, 9, 11, 14)$
- 18 Explain 4 bit binary adder / subtractor and draw necessary diagram.
- 19 Explain the working of J-K master-slave flip flop.
- 20 Discuss with necessary block diagram, the working of successive approximation