

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)

BSc DEGREE EXAMINATION MAY 2024
(Third Semester)

Branch – ELECTRONICS

DIGITAL ELECTRONICS/ DIGITAL PRINCIPLES & APPLICATIONS

Time: Three Hours

Maximum: 50 Marks

SECTION-A (5 Marks)

Answer ALL questions

ALL questions carry EQUAL marks

(5 x 1 = 5)

1. The decimal value of $(1000)_2$ is _____
i)1000 ii)8 iii)101 iv)16
2. The given Boolean expression is $Y = A\bar{B} + \bar{A}B$; if $A = 1$ and $B = 1$, then $Y =$ _____
i)1 ii)0 iii)1 and 0 iv)None
3. A Demultiplexer can be used to realize a _____.
i)Counter ii)Shift register
iii)Combinational circuit iv)Display system
4. Master-Slave configuration is used in flip-flops to _____.
i)Increase its clocking rate ii)Reduce power dissipation
iii)Elimination race-around condition iv)Improve its reliability
5. The main advantage of the successive – approximation method is _____.
i)Speed ii)Accuracy
iii)Resolution iv)None of these

SECTION - B (15 Marks)

Answer ALL Questions

ALL Questions Carry EQUAL Marks

(5 x 3 = 15)

6. a Explain 1's and 2's complement.
OR
b Explain the procedure for BCD addition.
7. a Analyze the term Pair, Quad and Octet in k-map with examples.
OR
b State and prove Demorgan's theorems.
8. a Draw the circuit and explain 4 bit parallel binary adder.
OR
b Explain the multiplexer with neat diagram.
9. a What is racing in J-K flip flop? Explain.
OR
b What are shift-register? Give its uses.
10. a Explain the operation of a 4-bit binary ladder with necessary circuit.
OR
b Explain the principle of A/D converter.

Cont...

SECTION -C (30 Marks)Answer **ALL** questions**ALL** questions carry **EQUAL** Marks

(5 x 6 = 30)

11 a Convert the following hexadecimal numbers to decimal

- i) $(E9)_{16}$
- ii) $(3FC.8)_{16}$
- iii) $(FFFF)_{16}$

OR

b Discuss about the excess – 3 code and explain.

12 a What is an XOR gate? Write its truth table and realize it using AND, OR and NOT gates.

OR

b Simplify using karnaugh map

$$Y = F(A,B,C,D) = \sum(0,1,2,4,5,10,11,14,15)$$

13 a Construct half adder and full adder circuits and draw their truth tables.

OR

b Explain the function of encoders with neat diagrams.

14 a Explain RS flip-flop and SR flip flop using NOR gates.

OR

b Explain about the operation of Up/Down counter.

15 a Explain about resistive divider type of D/A converter.

OR

b Explain about dual slope A/D converter.

Z-Z-Z

END