

PSG COLLEGE OF ARTS & SCIENCE  
(AUTONOMOUS)

BSc DEGREE EXAMINATION MAY 2024  
(Third Semester)

Branch – INFORMATION TECHNOLOGY

FUNDAMENTALS OF DIGITAL COMPUTERS

Time: Three Hours

Maximum: 50 Marks

**SECTION-A (5 Marks)**

Answer ALL questions

ALL questions carry EQUAL marks

(5 x 1 = 5)

- 1 What is the value of  $(1101)_2$  in decimal number system?  
(i)  $(13)_{10}$  (ii)  $(12)_{10}$   
(iii)  $(10)_{10}$  (iv)  $(15)_{10}$
- 2 The karnaugh map (K-map) technique provides a systematic method for simplifying \_\_\_\_\_.  
(i) Multiplexers (ii) Logic Gates  
(iii) Counters (iv) Boolean expression
- 3 The number of inputs in a half adder is \_\_\_\_\_.  
(i) 8 (ii) 2  
(iii) 11 (iv) 32
- 4 Which of the following is not a sequential circuit?  
(i) Flip flop (ii) Counter  
(iii) Shift register (iv) Multiplexer
- 5 The fastest data access is provided using \_\_\_\_\_.  
(i) Cache (ii) DRAM's  
(iii) SRAM's (iv) Registers

**SECTION - B (15 Marks)**

Answer ALL Questions

ALL Questions Carry EQUAL Marks

(5 x 3 = 15)

- 6 a Write short notes on binary codes.  
OR  
b Discuss the binary logic operations with its truth table.
- 7 a State the duality principle.  
OR  
b Justify the graphic symbols of NAND & NOR gate.
- 8 a Write short notes on full adder.  
OR  
b Bring out the neat sketch for design BCD to decimal decoder.
- 9 a Describe the block diagram for sequential circuit.  
OR  
b Discuss the functions used in shift register.
- 10 a Classify the modes of data transfer.  
OR  
b Distinguish RAM and ROM.

Cont...

**SECTION -C (30 Marks)**

Answer ALL questions

ALL questions carry EQUAL Marks

(5 x 6 = 30)

11 a Convert the following:

(i)  $(673.124)_8 = (?)_2$

(ii)  $(306.D)_{16} = (?)_2$

OR

b Classify the symbols for circuit of logic gates.

12 a Point out the axiomatic definition of Boolean algebra.

OR

b Simplify the Boolean function:

$$F(W,X,Y,Z) = \sum(0,1,2,4,5,6,8,9,12,13,14)$$

13 a Implement a full subtractor with two half subtractor and an OR gate.

OR

b Explain the block diagram of BCD Adder.

14 a Briefly explain the triggering of flip flops.

OR

b Distinguish synchronous counters with ripple counters.

15 a Compare synchronous and asynchronous data transfer.

OR

b Highlight the relationship between address and memory space in a virtual memory system.

Z-Z-Z

END