

**PSG COLLEGE OF ARTS & SCIENCE  
(AUTONOMOUS)**

**BSc DEGREE EXAMINATION MAY 2022  
(First Semester)**

Branch - ELECTRONICS

**CIRCUIT ANALYSIS**

Time: Three Hours

Maximum: 75 Marks

**SECTION-A (20 Marks)**

Answer ALL questions

ALL questions carry EQUAL marks

$(10 \times 2 = 20)$

- 1 Define Voltage
- 2 State the SI unit for Inductance and capacitance
- 3 Define Node
- 4 State Kirch off's II Law
- 5 What is Resonance ?
- 6 List the components of Resonance Circuit.
- 7 Draw the Purely resistive circuit
- 8 Define True Power.
- 9 Mention the use of Wattmeter.
- 10 Define Cycle.


**SECTION - B (25 Marks)**

Answer ALL questions

ALL questions carry EQUAL Marks

$(5 \times 5 = 25)$

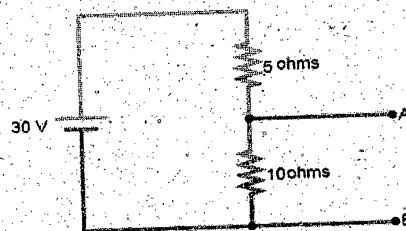
- 11 a Discuss about the Power and Energy.  
**OR**  
b Calculate the Voltage across the  $10\Omega$  resistor



- 12 a Explain the process of Mesh Analysis  
**OR**  
b State the Millman's theorem and give its uses in circuit analysis
- 13 a Calculate the time period of 30 Hz Sine wave  
**OR**  
b Explain the Angular relation of a sine wave.
- 14 a Discuss about Average Power.  
**OR**

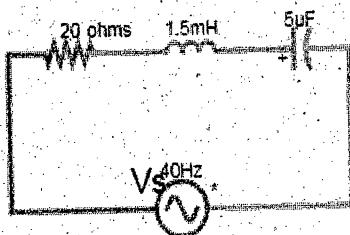**Cont...**

b Calculate the resonant frequency for the given circuit



15 a Explain the operation of Poly-phase

OR

b Discuss how the power is measured in 3 phase circuits.


**SECTION -C (30 Marks)**

Answer ANY THREE questions  
ALL questions carry EQUAL Marks

(3 x 10 = 30)

16. State and derive the equation for Ohm's Law.

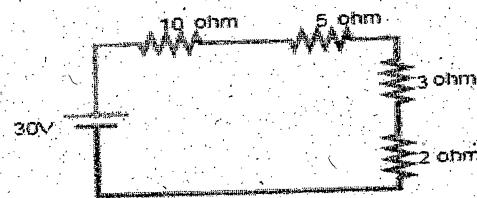17. Determine the total amount of power in the given circuit.



18. Elucidate the working of RLC series circuit.

19. Explain the Q factor of Parallel resonance

20. Describe the generation and advantages of 3-phase system

Z-Z-Z

END