

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)
BCA DEGREE EXAMINATION DECEMBER 2019
(First Semester)

Branch - COMPUTER APPLICATIONS

COMPUTER SYSTEM ARCHITECTURE

Time: Three Hours

Maximum: 75 Marks

SECTION-A (10 Marks)

Answer ALL questions

ALL questions carry EQUAL marks (10 x 1 = 10)

Numbers are represented in digital computer through a J _____ .

- (i) Binary operation (ii) Arithmetic operation
(iii) Binary code (iv) Digital operation

The basic logic gate whose output is the complement of the input is the

- (i) OR gate (ii) AND gate
(iii) INVERTER gate (iv) XOR gate

Boolean algebra does not have _____ inverses.

- (i) Boolean (ii) Additive
(iii) Complement (iv) Universe

Total number of Min terms in Three variable map is

- (i) 4 (ii) 3
(iii) 8 (iv) 5

Complements are used in digital computers for simplifying _____ operation.

- (i) subtraction (ii) addition
(iii) multiplication (iv) division

A half adder circuits need two binary inputs and _____ binary outputs.

- (i) one (ii) two
(iii) three (iv) four

There are _____ main types of sequential circuit,

- (i) zero (ii) one
(iii) two (iv) three

An n-bit register has a group of _____ flip flop.

- (i) n (ii) n+1
(iii) n-1 (iv) n+2

Status bit conditions are sometimes called as

- (i) zero bits (ii) flag bits
(iii) binary bits (iv) both (i) & (ii)

10 In immediate addressing mode _____ is given in instruction itself.

- (i) address (ii) code
(iii) data (iv) op code

SECTION - B (25 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks (5 x 5 = 25)

- 11 a Explain Gray code with example.
OR
b. Discuss the NAND operation.
- 12 a Explain the functions of Encoder.
OR
b Write note on Don't care condition.
- 13 a Explain RS flip flop with truth table.
OR
b Describe Binary addition with example.
- 14 a Write notes on synchronous counters.
OR
b Describe the function of Ring counter.
- 15 a Explain -Instrijption formats.
OR
b Write notes on 1-0 processor.

SECTION -C (40 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks (5 x 8 = 40)

- 16 a Explain OR gate with truth table.
OR
b Discuss about moving and storing information.
- 17 a Explain sum of product with suitable example.
OR
b Describe the function of De Multiplexers with truth table.
- 18 a Discuss the Edge Triggered R S flip flop.
OR
b Illustrate the Binary Subtraction with example.
- 19 a Describe the function of 54/74198 shift register with logic diagram.
OR
b Build logic diagram and describe the function of MOD3 counter.
- 20 a Discuss about the Stack Organization with diagram.
OR
b Briefly Explain Asynchronous Data transfer.