

**PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)
BSc DEGREE EXAMINATION MAY 2018
(First Semester)**

Branch- **ELECTRONICS**

CIRCUIT ANALYSIS

Time ; Three Hours

Maximum 75 Marks

SECTION-A (20 Marks!)

Answer **ALL** questions

ALL questions earn EQUAL marks

(10 x 2 = 20)

- 1 Explain the common colorcode for resistance,
- 2 Classify the resistors.
- 3 State Kirchoffs voltage law.
- 4 State Norton's theorem.
- 5 Give the relation between mean and peak value of an AC.
- 6 What is the time constant for RC circuit?
- 7 Define average power.
- 8 What is parallel Resonance?
- 9 What is transient response?
- 10 What are the advantages of three phase system?

SECTION - B (25 Marks)

Answer **ALL** Questions

ALL Questions Carry EQUAL Marks (5 x 5 = 25)

- 11 a Explain the series and parallel combination of resistors.
OR
b Explain about Star to Delta transformations.
- 12 a State and explain superposition theorem.
OR
b State and prove Thevenin's theorem.
- 13 a Explain about series RL circuit.
OR
b With suitable diagram explain pure capacitive circuit.
- 14 a State the concept of band width of a series RLC circuit,
OR
b Explain with a neat diagram for a series resonance.
- 15 a Explain about generation of three phase voltages.
OR
b Explain with neat diagram power measurement in a Single phase circuit by Wattmeter.

SECTION - C (30 Marks)

Answer any **THREE** Questions

ALL Questions Carry EQUAL Marks (3 x 10 = 30)

- 16 Illustrate the resistors color coding and give its value.
- 17 State and explain Superposition theorem.
- 18 With neat sketches explain RC series circuit.
- 19 Explain that how to derive Q factor of parallel resonance.
- 20 Explain the three Wattmeter method of measuring power in 3-phase circuits with neat sketch.